

Total No. of Questions : 6]

Roll No. 2282300078

[Total No. of Printed Pages : 3

**EW-71**

**B.Tech. I<sup>st</sup> Semester (CSE, IT & Electronics)**

**Examination, 2021-22**

**Basic Electronics Engineering**

**Paper - BE - 105**

**Time : 3 Hours]**

**[Maximum Marks : 60**

**Note : -Ques. No. 1 is compulsory. Attempt any two parts from  
Ques. No. 2 to Ques. No. 6.**

**1. Write short answers :**

**EW-71**

**(1)**

**P.T.O.**

- (i) Define barrier potential. What is its importance ?
  - (ii) What is the basic principle of operation of varactor diode
  - (iii) Name three region of operation in BJT. and mention corresponding applications.
  - (iv) Give ideal characteristics of OP-AMP.
  - (v) Where do we use storage oscilloscope ?
2. (a) Based on energy band theory of crystal differentiate between metals, semiconductors and insulators.
  - (b) With the help of VI characteristics curves. Explain the behaviour of ideal and practical diode.
  - (c) Describe junction capacitances of a semiconductor diode.
3. (a) Explain the principle of operation of light emitting diode.
  - (b) Compare half wave, full wave and bridge rectifier based on different parameters.
  - (c) Write short note on Tunnel diode.
4. (a) Discuss input and output characteristics of CE configuration and show the effect of Early effect on the characteristics curves.

- (b) Why is biasing required in BJT circuits ? Discuss voltage divider biasing circuit.
  - (c) Draw the physical structure of JFET and Explain its operation.
5. (a) What are multivibrators. Give its classification and applications.
- (b) Draw and explain zero crossing detector circuit of OP-AMP in both inverting and non-inverting mode.
  - (c) Discuss the working of 555 timer in Astable mode.
6. (a) Describe deflection and focussing system of CRO.
- (b) Write short note on LVDT.
  - (c) Explain the working of sampling oscilloscope with its block diagram.

\*\*\*