

Roll No. 2382306084

Total No. of Questions : 6]

[Total No. of Printed Pages : 8

EXS-85

B.Tech. IInd Semester (CSE, IT & Elect.)

Examination, 2023

Basic Electrical Engineering

Paper - BE-202

Time : 3 Hours]

[Maximum Marks : 60

- Note :-** (i) Q. 1 is MCQ based questions. Each objective question carry one mark each.
- (ii) Attempt all questions, internal choice is given. Each question carries 10 marks.
- (iii) All parts of each question are to be attempted at

EXS-85

(1)

one place.

(iv) Explain through sketches wherever possible.

1. Choose the correct one :

(i) Kirchhoff's laws are useful in determining-

- ☒ (a) Current flowing in a circuit
- (b) EMFs and Voltage drops in a circuit
- (c) Power in a circuit
- (d) All the above

(ii) Three resistance 14.5Ω , 25.5Ω and 60Ω are connected in series across 200 V. What will be the voltage drop across 14.5Ω .

- ☒ (a) 29 V
- (b) 13.5 V
- (c) 14 V
- (d) 18 V

(iii) The unit of frequency is-

- (a) Cycle

- (b) Cycle-second
 - (c) Hertz second
 - ~~(d)~~ Hartz
- (iv) In an AC circuit (sine wave) with R and L in series.
- (a) Voltage across R and L 180° out of phase
 - ~~(b)~~ The voltage across R lags the voltage across L by 90°
 - (c) The voltage across R leads the voltage across L by 90°
 - (d) Voltage across R and L are in phase
- (v) Transformer is-
- (a) a device used to convert low alternating voltage to a high alternating voltage
 - ~~(b)~~ a device used to convert alternating current to direct current
 - (c) a device used to convert low alternating current to a high alternating current

- (d) used only for low alternating voltage.
- (vi) The purpose of the transformer core is to provide
- (a) Low reluctance path
 - (b) High inductive path
 - (c) High capacitive path
 - (d) High reluctance path
- (vii) The output power of any electrical motor is taken from the
- (a) Armature
 - (b) Field
 - (c) coupling method on shaft
 - (d) motor frame
- (viii) What is the lamination used for the stator of induction motor?
- (a) cast iron
 - (b) die cast aluminum alloy frame
 - (c) cast iron or die cast aluminum alloy frame

(d) cast iron and die cast aluminum alloy frame

(ix) In a pure inductive circuit.

- (a) The current is in phase with the voltage
- (b) The current lags behind the voltage by 90°
- (c) The current leads the voltage by 90°
- (d) The current can lead or lag by 90°


(x) Armature reaction of an unsaturated D.C. machine is-

- (a) Cross-magnetizing
- (b) Demagnetizing
- (c) Magnetizing
- (d) None of above

2. (a) Explain the advantages and disadvantages of power system?
- (b) Describe different types of power system?

OR

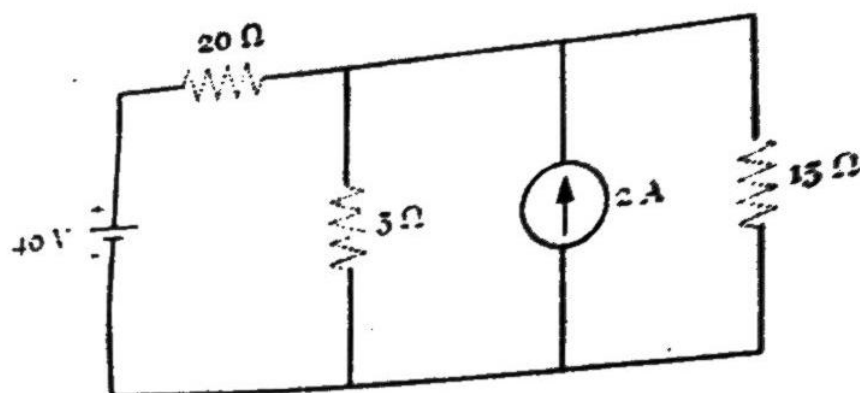- (a) Solve the given circuit to find the current through $15\ \Omega$ using Thevenin's Theorem.



- (b) Explain star to delta and delta to star transformation of resistances with neat diagram.
3. (a) Explain the power measurement of three phase ac circuit using 2 wattmeter method.
- (b) Write the equation for series RLC circuit with the proper diagram, phasor diagram and power equations.

OR

- (a) Explain the Concept of phasor & Concept of Power factor using any suitable example.
- (b) Derive the expression of power in R-L circuit. Draw the phasor diagram too.

4. (a) Explain about hysteresis and eddy current losses in transformer?
- (b) Explain about open circuit and short circuit tests in single phase transformer.

OR

- (a) Explain the self & mutual inductances Explain the leakage & Fringing of flux?
- (b) Explain the working principle of Transformer. Derive an expression for the emf induced in Transformer.
- (a) Explain the working principle and construction of D.C. machine.
- (b) A six-pole lap wound generator has 720 conductors, a flux of 40 mWb per pole is driven at 400 rpm. Find the generated emf.

OR

- (a) Compare induction machine and synchronous machine on the basis of construction and application.

- (b) Explain the basic working principle of induction machine and types of induction machine.

6. Write short notes on :

- (a) Smart Grid
- (b) Load & its characteristics

OR

- (a) Explain the structure of Power System
- (b) Write short notes on micro grid