

Roll No.

Total No. of Questions : 6]

[Total No. of Printed Pages : 5

EX-73

B.Tech. Ist Semester (CSE, IT & Electronics)

Examination, 2022-23

Basic Electronics Engineering

Paper - BE - 105

Time : 3 Hours]

[Maximum Marks : 60

**Note : -Ques. No. 1 is compulsory. Attempt any two parts from
Ques. No. 2 to Ques. No. 6.**


1. Write short answers :

EX-73

(1)

P.T.O.

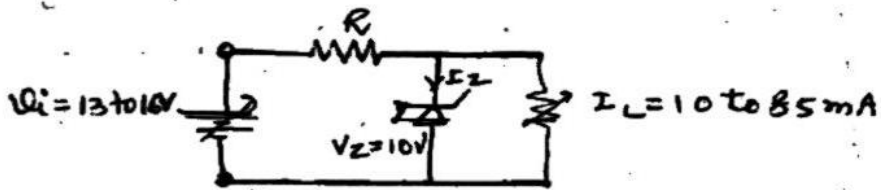- (i) Define junction capacitances of a diode.
 - (ii) What is the principle of operation of LED ?
 - (iii) What is early effect ?
 - (iv) Define and classify multivibrator circuits.
 - (v) Classify transducess.
2. (a) Define the following.
- (i) Intrinsic and extrinsic semiconductors.
 - (ii) Depletion region and barrier potential.
- (b) Discuss the working of P-N junction diode in forward and reversebias. Explain how and why breakdown occurs.
- (c) Explain the construction and working of point contact diode.
3. (a) Find the value of R in the following circuit of a zener regulator.





Also give the difference between zener and avalanche break down.

(b) Compare all the rectifier circuits based on.

- (i) PIV
- (ii) Ripple factor
- (iii) Efficiency
- (iv) Output waveform
- (v) Circuit

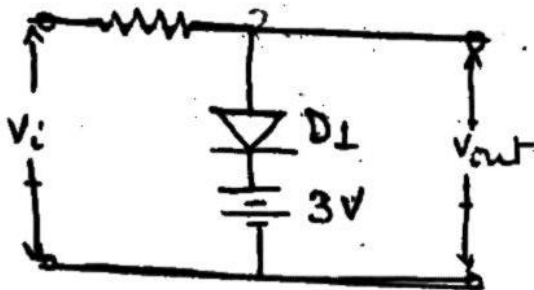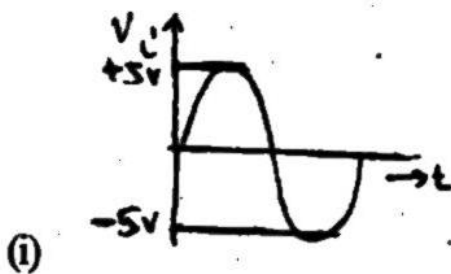
(c) Draw o/p waveform (V_{out}) for the following circuits. When $D1$ is an ideal diode. Explain the working of the circuits.



EX-73

(3)

P.T.O.

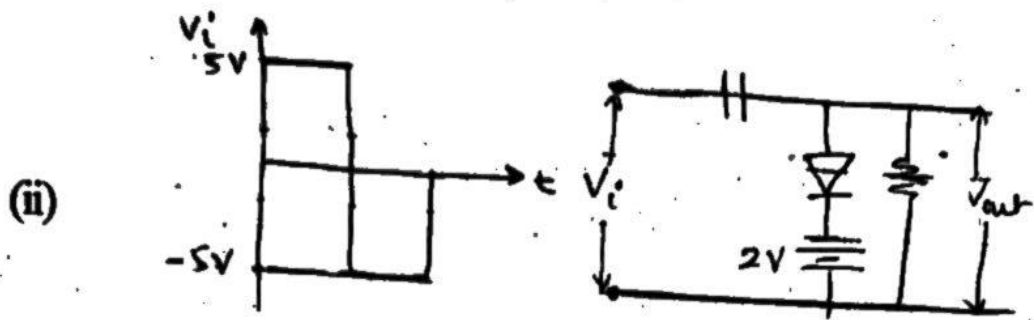

4. (a) With the help of input and output characteristics curves of CE configuration in BJT, Explain different region of operation.
 - (b) Why is biasing required in BJT ? Explain with diagram voltage divider Biasing circuit.
 - (c) Discuss the working of MOSFET. A/So give its constructional features.
5. (a) Describe the working of IC 555 timer in Astable mode. Give its applications.
 - (b) Derive the gain formula for op-AMP in inverting and non inverting mode.
 - (c) Write short note on schmitt trigger circuit.

6. (a) Explain the principle of operation of strain guage. Define guage factor.
- (b) Draw the block diagram of CRO and Explain in detail deflection and focussing system.
- (c) Explain the working of sampling oscilloscope with suitable block diagram.

AJEET SONI

