

Roll No.

Total No. of Questions : 6]

[Total No. of Printed Pages : 10

EX-85

B.Tech. IInd Semester (CSE, IT & Elect.)

Examination, 2022-23

Basic Electronics Engineering

Paper - BE-202

Time : 3 Hours]

[Maximum Marks : 60.

Note :- Scientific calculator is required. All parts in question no. 1

are compulsory, internal choice is given in other questions.

All parts of a question/section should be answered at
one place.

EX-85

(1)

P.T.O.

1. Choose any one :

- (i) Identify the passive elements among the following
- (a) Voltage Source
 - (b) Current Source
 - (c) Inductor
 - (d) Transistor
- (ii) The Reciprocity Theorem is applicable for ____
- (a) Single-source networks
 - (b) Multi-source networks
 - (c) Both single and Multi-source networks
 - (d) Neither single nor multi-source networks
- (iii) A circuit of a resistance R in series with a capacitive reactance of 60Ω . Determine the value of R for which the power factor of the circuit is 0.8.

EX-85

(2)

(a) 45Ω

(b) 60Ω

(c) 80Ω

(d) 75Ω

- (iv) In a delta connected system, the expression of power (P) is ?

(a) $V_L I_L \cos \phi W$

(b) $\sqrt{3} V_L I_L \cos \phi W$

(c) $3 V_L I_L \cos \phi W$

(d) $3\sqrt{3} V_L I_L \cos \phi W$

- (v) The inductive reactance of a transformer depends on

(a) Electromotive force

(b) Magnetomotive force

(c) Magnetic flux

(d) Leakage flux

EX-85

(3)

(vi) The unit of magnetic flux is -

- (a) Henry
- (b) Weber
- (c) Ampere turn/mT
- (d) Ampere/meter

(vii) The speed of a 4-pole, 60Hz synchronous machine will be

- (a) 1800 rpm
- (b) 2400 rpm
- (c) 3000 rpm
- (d) 3600 rpm

(viii) The slip of an induction motor does not depend on -

- (a) Rotor speed
- (b) Synchronous speed
- (c) Shaft torque

EX-85

(4)

(d) Core loss component

(ix) For a 6-pole wave wound DC generator the number of parallel path will be -

- (a) 12
- (b) 6
- (c) 4
- (d) 2

(x) The segments of the commutator of a DC machine are made of


- (a) Brass
- (b) Copper
- (c) Carbon
- (d) Silicon steel

2. (a) Determine the current through each branch using Maxwell's loop method in Fig. 1.

EX-85

(5)

P.T.O.

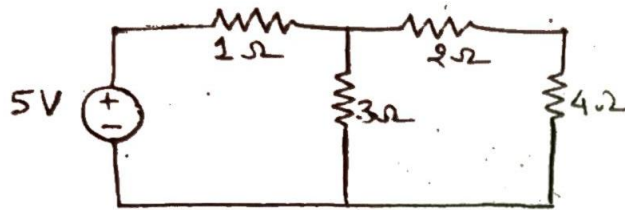

- (b) State and explain Thevenin's Theorem.

OR

- (a) Develop the relation for star-delta conversion.
- (b) Explain the Structure of Electrical Power System.
3. (a) A coil of resistance $40\ \Omega$ and inductance 0.75 H form part of a series circuit for which the resonant frequency is 55 Hz . If the supply voltage is 250 V , 50 Hz , find the following-

- (i) the line current,

EX-85

(6)

- (ii) the power factor,
- (iii) the voltage across the coil.

- (b) Derive the expression for current and power in pure resistive and pure inductive circuits.

OR

- (a) Two wattmeters are used for measuring the power input and power factor of an over-excited synchronous motor. If the readings of meters are -2.0 kW and 7.0 kW respectively, calculate the input and power factor of motor.
- (b) What is an admittance triangle? Define all the three components along with formulas involved.
4. (a) Two coils are wound on a magnetic circuit of 50 sq.cm . cross section and mean length of 100 cm . One coil has

EX-85

(7)

P.T.O.

80 turns and other has 700 turns. Calculate the mutual inductance of the coils, if the relative permeability of iron path is 1500.

- (b) Derive the expression for dynamically induced emf.

OR

- (a) Define efficiency and voltage regulation of transformer.
(b) A 200 kVA, 2500/250V, 50 Hz single phase transformer gave the following results -

OC test (LV side) : 250 V, 1.5 Amp, 105 W

SC test (HV test) : 104 V, 8 Amp, 320 W.

Calculate the parameters of equivalent circuit of transformer to LV side, and draw the equivalent circuit.

5. (a) Derive an expression for generated emf in DC generator.

EX-85

(8)

- (b) Calculate the no load terminal voltage of a 3-phase, 4 pole, star connected alternator running at 1500 rpm, having flux per pole of 66 m Wb. The machine has 72 armature slots, 10 conductors per slot. The winding factor is 0.96.

OR

- (a) Develop an equivalent circuit of a 3-phase induction motor.
(b) The power input to a 230 V, DC shunt motor is 8.477 kW. The field resistance is $230\ \Omega$ and armature resistance is $0.28\ \Omega$. Find the input current, armature current and back emf.

6. (a) Explain the operating principle of circuit breaker.

EX-85

(9)

P.T.O.

- (b) What do you understand by fault in a power system, explain ?

OR

- (a) What is the requirement of Power Grid ?
- (b) Explain the principle of Buchholz relay, also write its limitation.
